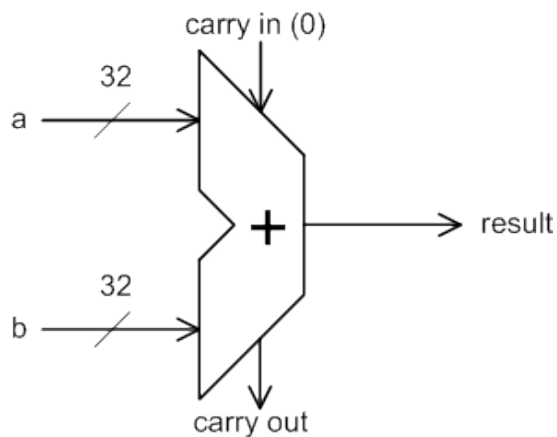


When N = 32

- If we use the two's complement method
 - 0000 0000 0000 0000 0000 0000 0000 0000 = 0
 - 0000 0000 0000 0000 0000 0000 0000 0001 = +1
 - 0000 0000 0000 0000 0000 0000 0000 0010 = +2
 - ...
 - 0111 1111 1111 1111 1111 1111 1111 1110 = +2,147,483,646
 - 0111 1111 1111 1111 1111 1111 1111 1111 = +2,147,483,647
 - 1000 0000 0000 0000 0000 0000 0000 0000 = - 2,147,483,648
 - 1000 0000 0000 0000 0000 0000 0000 0001 = - 2,147,483,647
 - 1000 0000 0000 0000 0000 0000 0000 0010 = - 2,147,483,646
 - ...
 - 1111 1111 1111 1111 1111 1111 1111 1101 = - 3
 - 1111 1111 1111 1111 1111 1111 1111 1110 = - 2
 - 1111 1111 1111 1111 1111 1111 1111 1111 = - 1

Addition

- We are quite familiar with adding two numbers in decimal
 - What about adding two binary numbers?
- If we use the two's complement method to represent binary numbers, addition can be done in a straightforward way



Suppose:

N=8

a=20


b=30

What is result and carry out?

Addition

- $N=8$, $a=20$, $b=30$
- Do binary addition to get result and carryout
- Convert A and B to binary? How?
 - $a=20=4+16=2^2+2^4 \Rightarrow a$ is 0001 0100b
 - $b=30=16+8+4+2=2^4+2^3+2^2+2^1 \Rightarrow b$ is 0001 1110b


NOTE: $N=8$ in this example

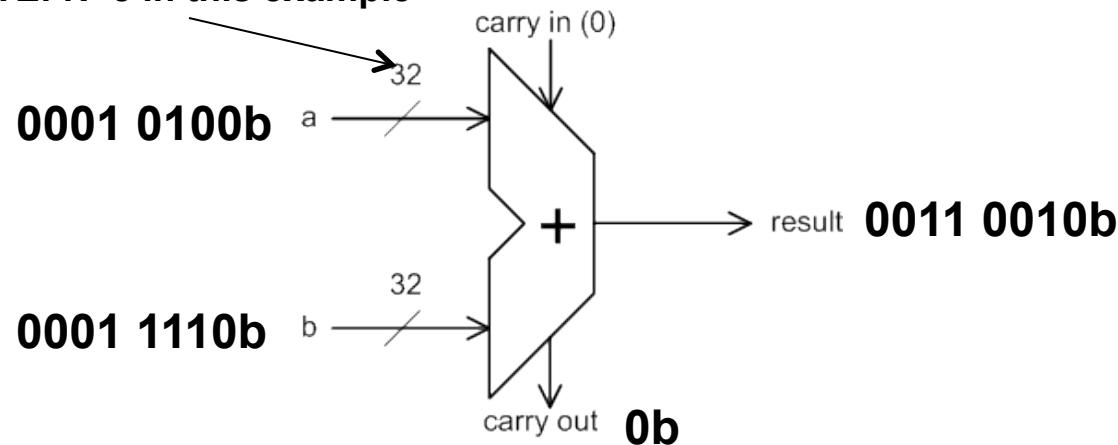

```
0001 0100b
+ 0001 1110b
-----
0 0011 0010b
```

Addition

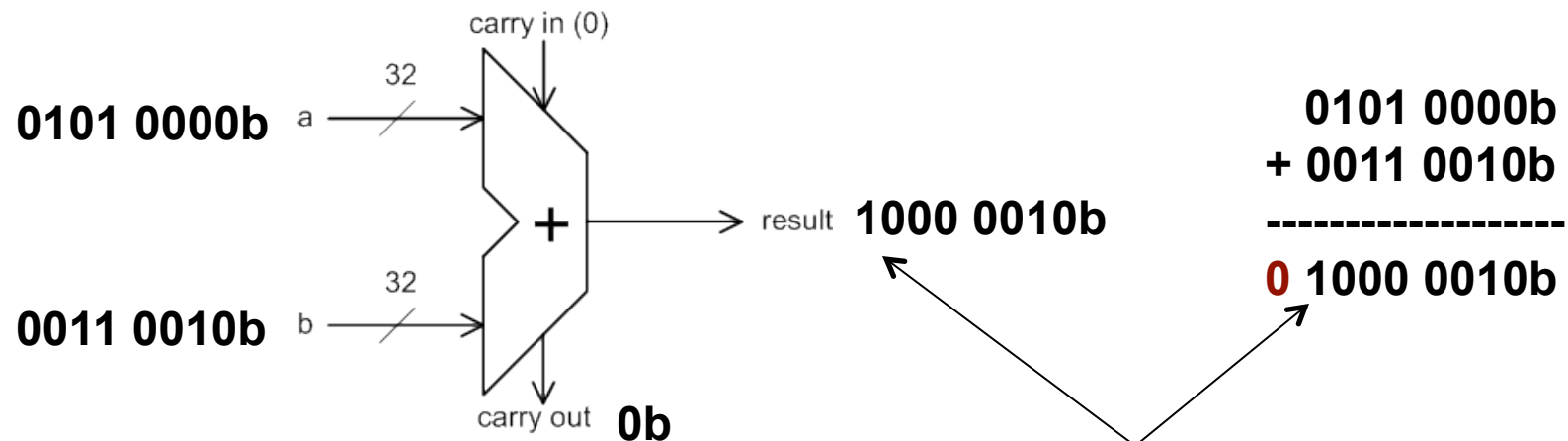- $N=8$, $a=80$, $b=50$
- Do binary addition to get result and carryout
- Convert A and B to binary? How?
 - $A=80=64+16=2^6+2^4 \Rightarrow a$ is 0101 0000b
 - $b=50=32+16+2=2^5+4^3+2^1 \Rightarrow b$ is 0011 0010b



Result is NEGATIVE!


Overflow

- Because we use a limited number of digits to represent a number, the result of an operation may not fit
- No overflow when result remains in expected range
 - We ***add two numbers with different signs***
 - We ***subtract a number from another number with the same sign***
- When can overflow happen?

| <u>a</u> | <u>b</u> | <u>overflow possible?</u> |
|----------|----------|---------------------------|
| + | + | yes |
| + | - | no |
| - | + | no |
| - | - | yes |

Overflow

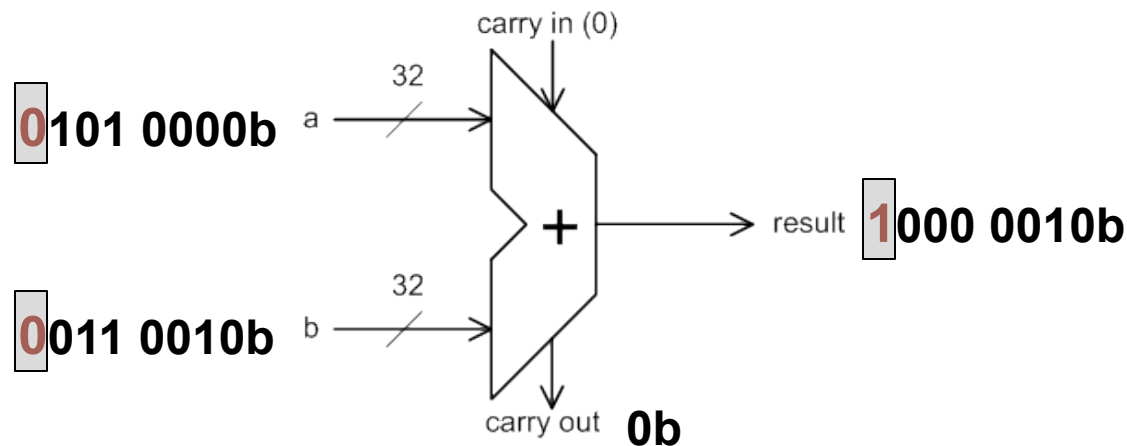- What is special about the cases where overflow happened?
 - The input values signs are the same; so, can go outside range*
- Overflow detection
 - Adding two positive numbers yields a negative number
 - Adding two negative numbers yields a positive number



Check signs
a is positive
b is positive
result isn't!

Overflow

- Can detect by inspecting sign bits of inputs and output
- Alternatively, can also detect by watching “carries”

```
0 1 1 1 0 0 0 0 x   (carries from previous bit add)
  0 1 0 1 0 0 0 0    a
+ 0 0 1 1 0 0 1 0    b
-----
0 1 0 0 0 0 1 0
```

Notice the carry into sign bit is different than the final carryout
When carry into sign bit doesn't equal carryout implies overflow

What happens on overflow?

- The CPU can
 - Generate an exception (what is an exception?)
 - Set a flag in the status register (what is the status register?)
 - Do nothing
- Languages may have different notions about overflow
- Do we have overflows in the case of unsigned, always positive numbers?
 - Example: `addu`, `addiu`, `subu`

MIPS example

- I looked at the MIPS32 instruction set manual
- ADD, ADDI instructions generate an ***exception*** on overflow
- ADDU, ADDIU are ***silent***

```
li    $t0, 0x40000000
add   $t1, $t0, $t0
```


← MARS give error

```
li    $t0, 0x40000000
addu  $t1, $t0, $t0
```

← MARS doesn't give error
\$t1=0x80000000


Subtraction

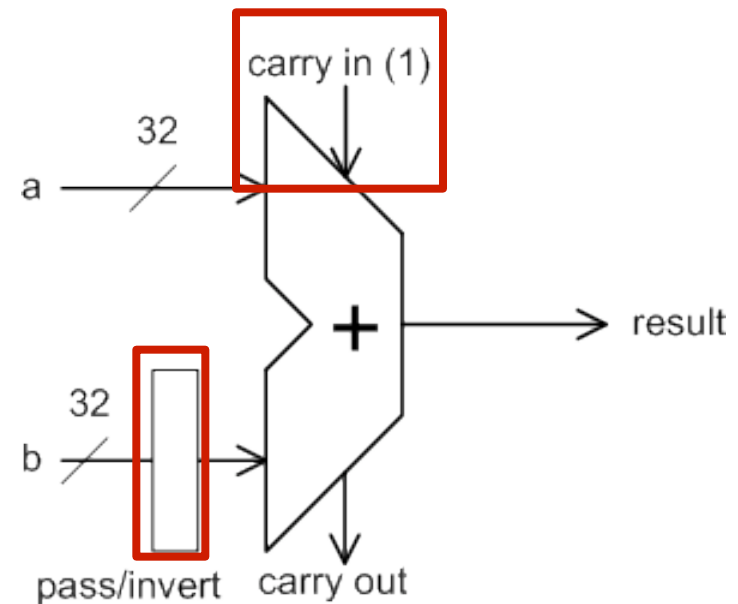- We know how to add
- We know how to negate a number
- We will use the above two known operations to perform subtraction
- $A - B = A + (-B)$
- The hardware used for addition can be extended to handle subtraction!



Subtraction

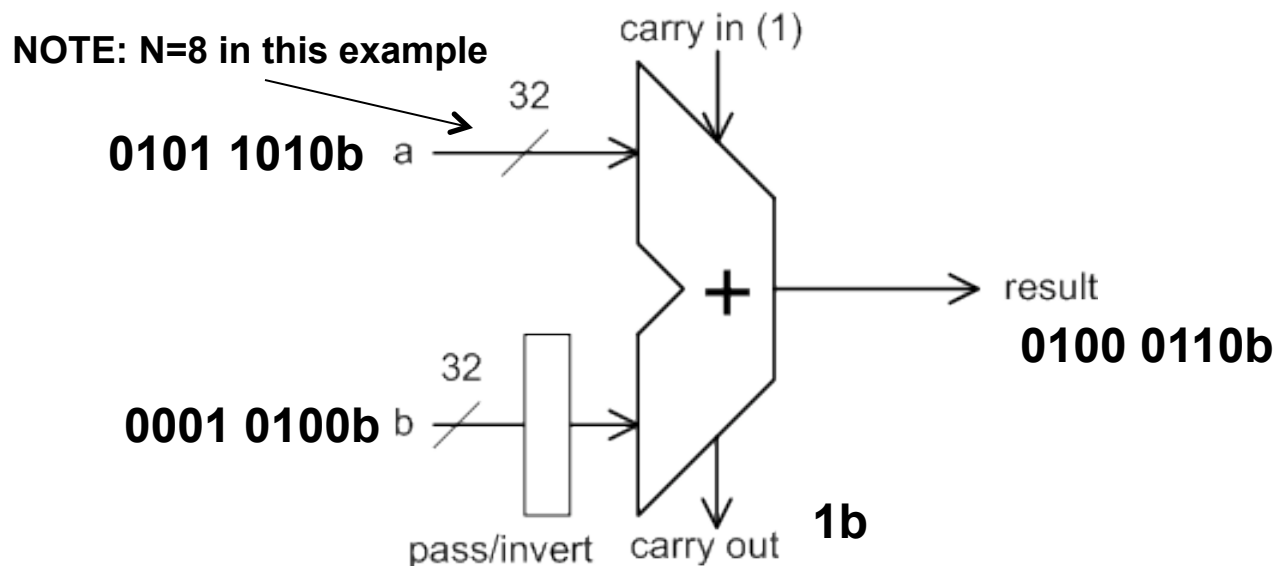- N=8, a=90, b=20
- Do binary subtraction ($A+(-B)$) to get result and carryout
- Convert A and B to binary? How?
 - a=90 is 0101 1010b
 - b=20 is 0001 0100b



find -b
 invert 0001 0100b
 = 1110 1011b
 + 0000 0001b


 1110 1100b

Now, add a
 0101 1010b
 + 1110 1100b

 1 0100 0110b

1-bit adder

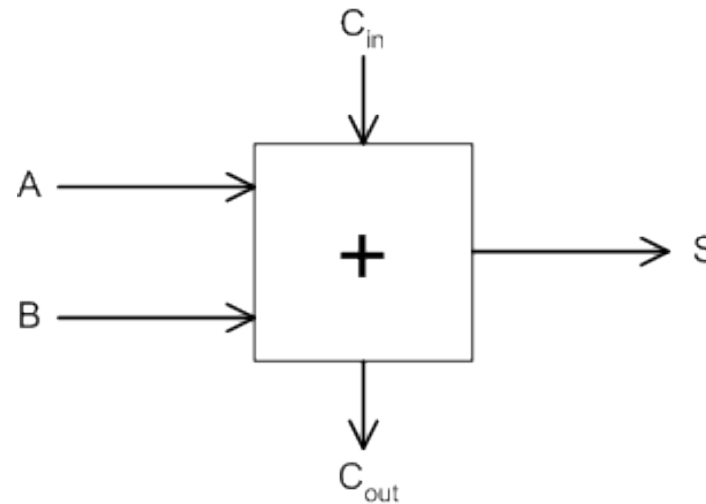
- We will look at a single-bit adder
 - Will build on this adder to design a 32-bit adder
- 3 inputs
 - A: 1st input
 - B: 2nd input
 - C_{in} : carry input
- 2 outputs
 - S: sum
 - C_{out} : carry out



1-bit adder

- What are the binary addition rules?

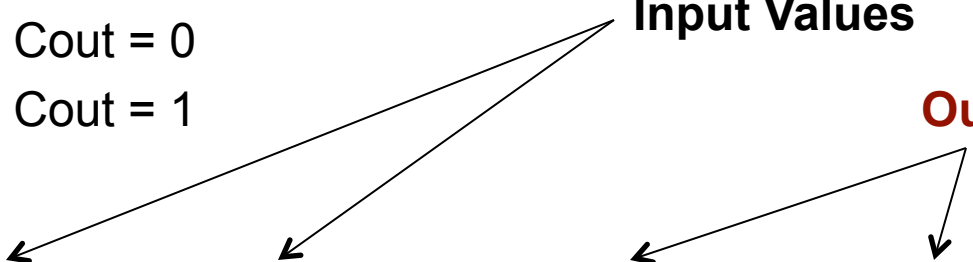- $0 + 0 = 0$, Cout = 0
- $0 + 1 = 1$, Cout = 0
- $1 + 0 = 1$, Cout = 0
- $1 + 1 = 0$, Cout = 1



| A | B | S | Cout |
|---|---|---|------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

1-bit adder

- What about Cin?

| A | B | Cin | S | Cout |
|---|---|-----|---|------|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |


1-bit adder

- What about Cin?

| A | B | Cin | S | Cout |
|---|---|-----|---|------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

N-bit adder

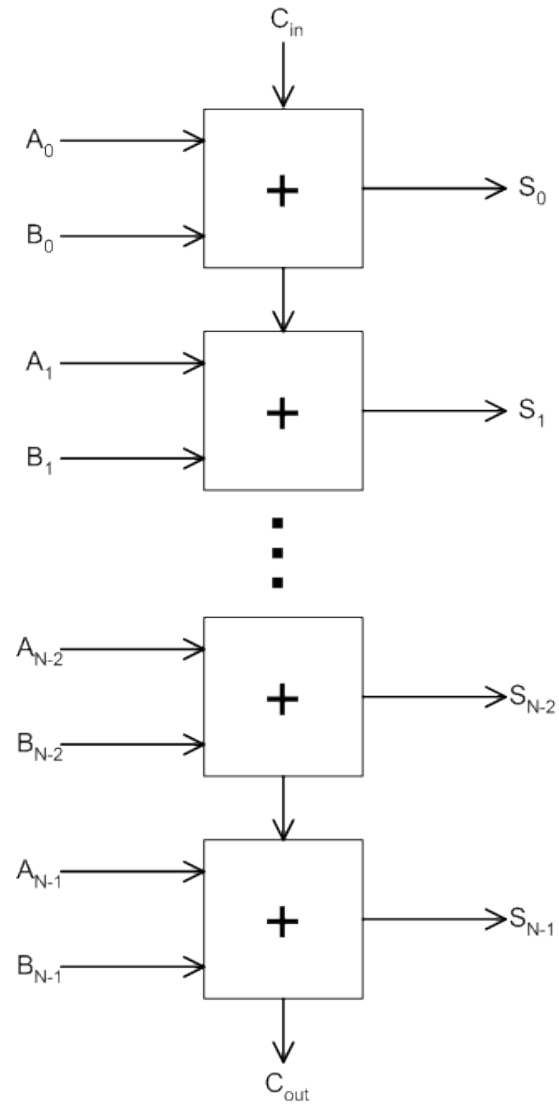- An N-bit adder can be constructed with N single-bit adders
 - A carry out generated in a stage is propagated to the next (“ripple-carry adder”)
- 3 inputs
 - A: N-bit, 1st input
 - B: N-bit, 2nd input
 - C_{in} : carry input
- 2 outputs
 - S: N-bit sum
 - C_{out} : carry out



N-bit ripple-carry adder

